Better Circuits For Boolean Functions

René Peralta National Institute of Standards and Technology

> Cybersecurity Innovation Forum September 2015

Circuits

- Binary operands $\{0,1\}$.
- Binary operations , e.g.

$$1 + 1 = 0$$

Circuits

Majority(a, b, c) = ab + ac + bc

Circuits

$\mathbf{Majority}(\mathbf{a},\mathbf{b},\mathbf{c}) = \mathbf{ab} + \mathbf{ac} + \mathbf{bc}$



Figure 1: Equivalent circuits over **GF(2)**.

• Number of gates;

- Depth;
- Number of multiplication gates (ANDS).

Optimality is out of reach

• Finding optimal circuits is NP-Hard or worse.

Optimality is out of reach

• Finding optimal circuits is NP-Hard or worse.

• We are interested in practical applications.

Optimality is out of reach

• Finding optimal circuits is NP-Hard or worse.

• We are interested in practical applications.

• Hence we are looking into the *concrete complexity* of circuit optimization problems.

 Platonic view: these objects are not "created" but discovered.

This is basic metrology

 Platonic view: these objects are not "created" but discovered.
Find, measure ...

This is basic metrology

 Platonic view: these objects are not "created" but discovered.
Find, measure ...

• Modern tool is the computer.

 Platonic view: these objects are not "created" but discovered.
Find, measure ...

• Modern tool is the computer.

 Not using our great computational power for this is like not using microscopes to determine the structure of living cells.

example: binary multiplication



Figure 2: 5 x 5 multiplication with optimal number of AND gates

Applications

Homomorphic Encryption

Cryptanalysis

Multiparty Computation

Privacy Preserving Proofs

Lightweight Crypto

Applications

Homomorphic Encryption

Cryptanalysis

Multiparty Computation

THANKS

Privacy Preserving Proofs

Lightweight Crypto